

Microcontroller Based Inductance Capacitance Meter



MUDIT AGARWAL

This is the Inductance / Capacitance Meters circuit. One can easily build this LC Meter measure inductances starting from 1mH to 100mH, 1 μ H to 1000 μ H, 10nH to 1000nH and capacitance from 0.1pF to 0.9 μ F. This inductance capacitance meter has Zero out switch that will reset the initial inductance capacitance, making sure that the final readings of the LC Meter are as accurate as possible. Further this Inductance Capacitance Meter circuit uses an auto ranging system, to come over the headache to select ranges manually. The resonance frequency of LC can be determined by using the frequency formula given below.

$$f_r = 1 / (2\pi \sqrt{LC})$$

Note that there are three variables that we can work with; f_r , L and C (f_r represents a frequency, L inductance and C capacitance). If we know the values of the two variables we may calculate the value of the third variable. For example if we want to determine the value of an unknown inductor with X inductance. We plug X inductance into the formula and we also use value of a known capacitor. Using this data we can calculate the frequency. Once we know the frequency we can use the power of the algebra and rewrite the above formula to solve for L (inductance). This time we will use the calculated frequency and a value of a known capacitor to calculate the inductance. We just calculated the value of unknown inductor, and we may use the same technique to solve for the unknown capacitance and even frequency.

The LC Meter uses a LM311 IC that functions as a frequency generator and this is exactly what we need. If we want to calculate the value of an unknown inductor we use a known 1000pF capacitor and the value of an unknown inductor. LM311 will generate a frequency that we can measure with a frequency meter. Once we have this information we can use the frequency formula to calculate the inductance. The same thing can be

done for calculating the value of a unknown capacitor. This time we don't know the value a capacitor so instead we use the value of a known inductor to calculate the frequency. Once we have that information we apply the formula to determine the capacitance.

All this sounds great, however if we want to determine the value of a lot of inductors / capacitors then this may become a very time consuming process. This circuit uses PIC16F84A microcontroller from microchip. PIC16F84A is like a small computer that can execute HEX programs that are written using an assembly language. PIC16F84A is a very flexible microcontroller. PIC16F84A IC requires very minimal number of external components like 4MHz crystal / resonator and few resistors depending on what project we are building. Before we can use PIC16F84A microchip we have to program it with a HEX code which has to be sent from the computer. In the next step we use the frequency generated by LM311 IC and pass it

Pins	Symbol	Function
1	Vee	Ground
2	Vdd	+5V
3	Vo	Contrast
4	RS	Register Select
5	RW	Read Write
6	En	Enable Signal
7	D0	Data Bit 0
8	D1	Data Bit 1
9	D2	Data Bit 2
10	D3	Data Bit 3
11	D4	Data Bit 4
12	D5	Data Bit 5
13	D6	Data Bit 6
14	D7	Data Bit 7
15	VA	Backlight +5V
16	VK	Backlight GND

Table 1.

CONSTRUCTION

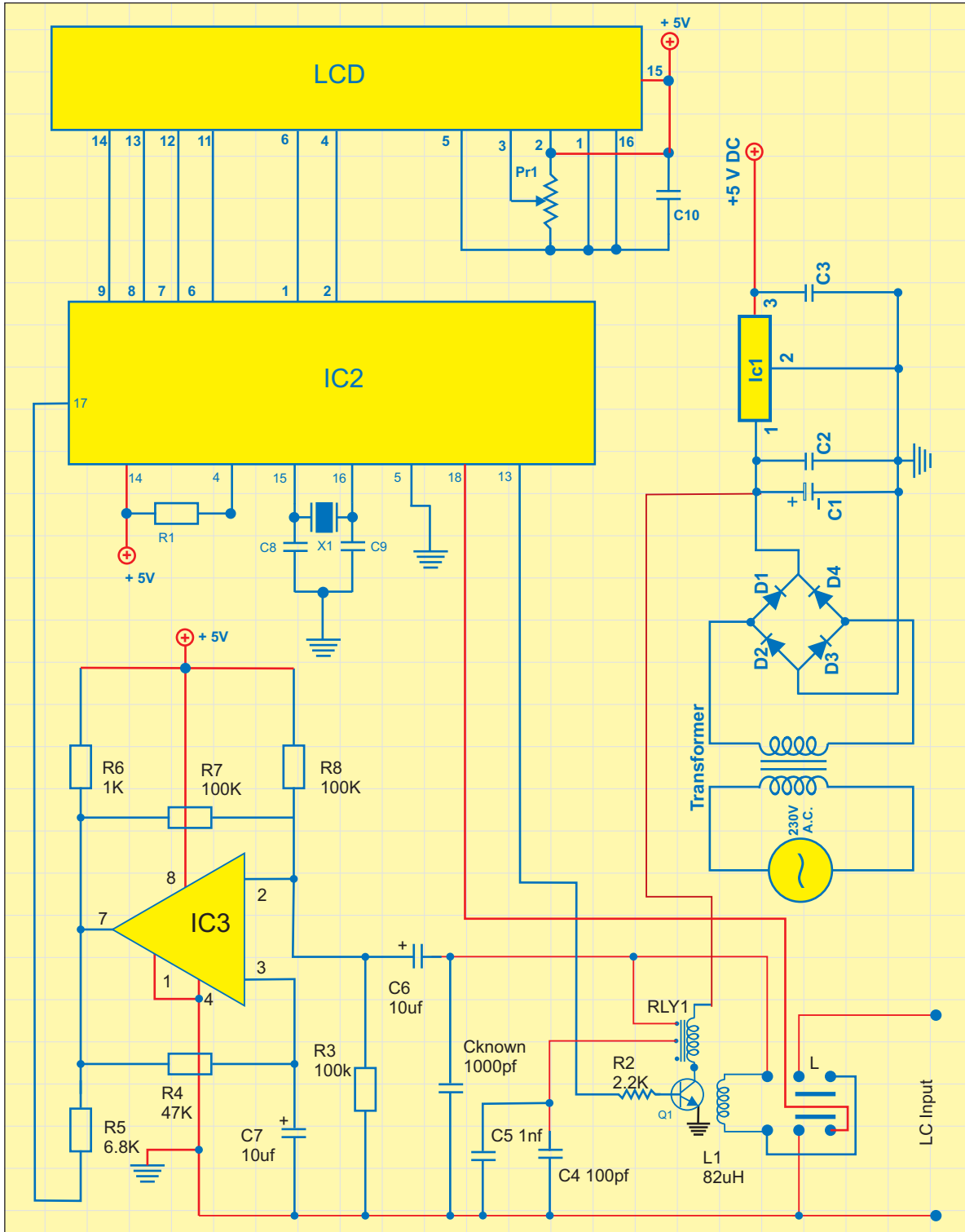


Fig.1 : Circuit Diagram of Microcontroller Based Inductance Capacitance Meter

on to PIC16F84A's PIN 17. We designate this pin as an input, as well as all other pins that are directly connected to switches and jumpers. User can use these inputs to tell the microchip to execute

specified set of instructions or perform calculations. Once the microchip will calculate the unknown inductance or capacitance it will use PINs that are designated as outputs and pass the results on to the

CONSTRUCTION

16 character LCD display. Most of the character LCD displays have 14 or 16 PINs. LCD with 14 pins donot have backlight. The LCD pins function is shown in table 1.

Software

```
list    p=pic16f84a
include p16f84a.inc
__config _hs_osc & _wdt_off &
_pwrte_on& _cp_off
c10m equ h'0c'
c01m equ h'0d'
c10s equ h'0e'
c01s equ h'0f'
lcd7_0 equ b'00110011'
lcd7_1 equ b'00110010'
lcd7_2 equ b'00111000'
lcd7_3 equ b'00001110'
lcd7_4 equ b'00000110'
lcd7_5 equ b'00001100'
lcd7_6 equ b'00100111'
lcd7_7 equ b'00000001'
lcd7_8 equ b'00100111'
lcd7_9 equ b'10000000'
lcd70 equ h'10'
lcd71 equ h'11'
lcd72 equ h'12'
lcd73 equ h'13'
lcd74 equ h'14'
lcd75 equ h'15'
lcd76 equ h'16'
lcd77 equ h'17'
lcd78 equ h'18'
```

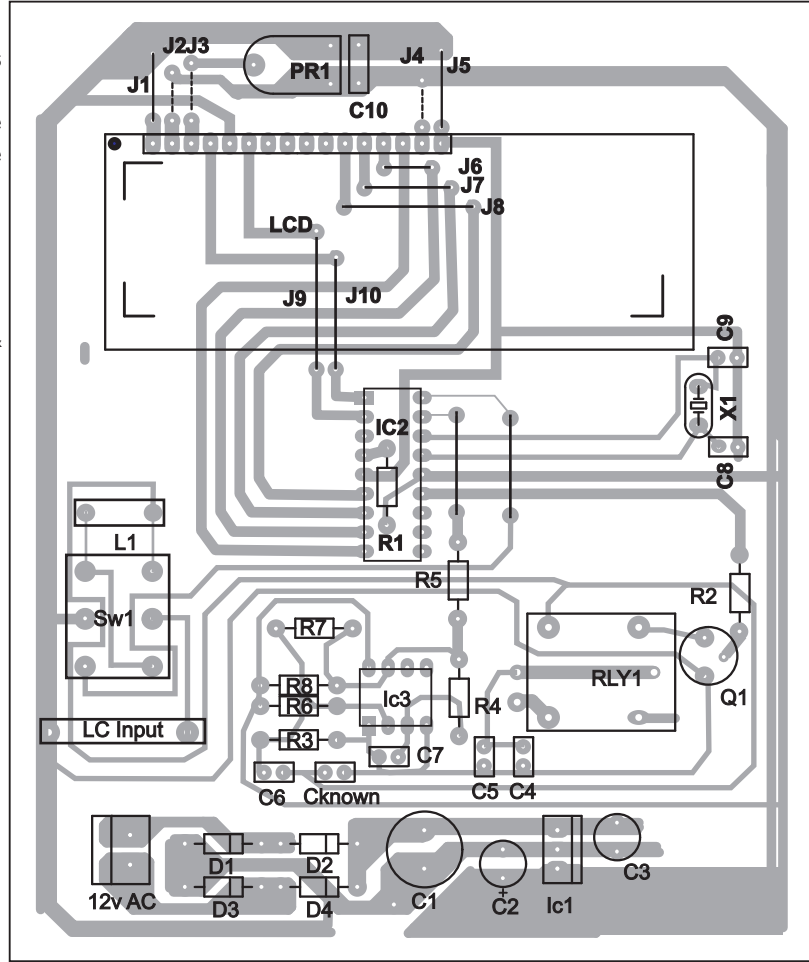


Fig.2: Component Layout o Microcontroller Based Inductance Capacitance Meter.

COMPONENT LIST

SEMICONDUCTOR DEVICES

IC1	7805
IC2	PIC16f84A
lc3	LM311
D1-D4	1N4007

CAPACITORS

C1	1000uf/25V
C2,C3,C10	0.1uf
C8,C9	22pf
C4	100pf
C5	1nf
C6,C7	10uf
Cknown	1000pf

RESISTORS

R1	10K
R2	2.2K
R3	100K
R4	47K
R5	6.8K
R6	1K
R7,R8	100K
Pr1	2K

MISCELLANEOUS

Transformer	12V
X1	4 MHZ
LCD	16X2 Liquid Crystal Display
Sw1	Double Pole Double Way Switch

```
lcd79 equ h'19'
tm_cnt equ h'1a'
time_f equ h'1b'
ttl_in equ h'1c'
w_save equ h'1d'
s_save equ h'1e'
cnt500u equ h'1f'
cnt1m equ h'20'
ra0 equ 0
ra1 equ 1
ra2 equ 2
ra3 equ 3
ra4 equ 4
rb6 equ 6
org 0
goto init
org 4
goto int
org 5
init
bsf status,rp0
movlw b'00010000'
movwf trisa
movlw b'00000111'
movwf option_reg
bcf status,rp0
```

CONSTRUCTION

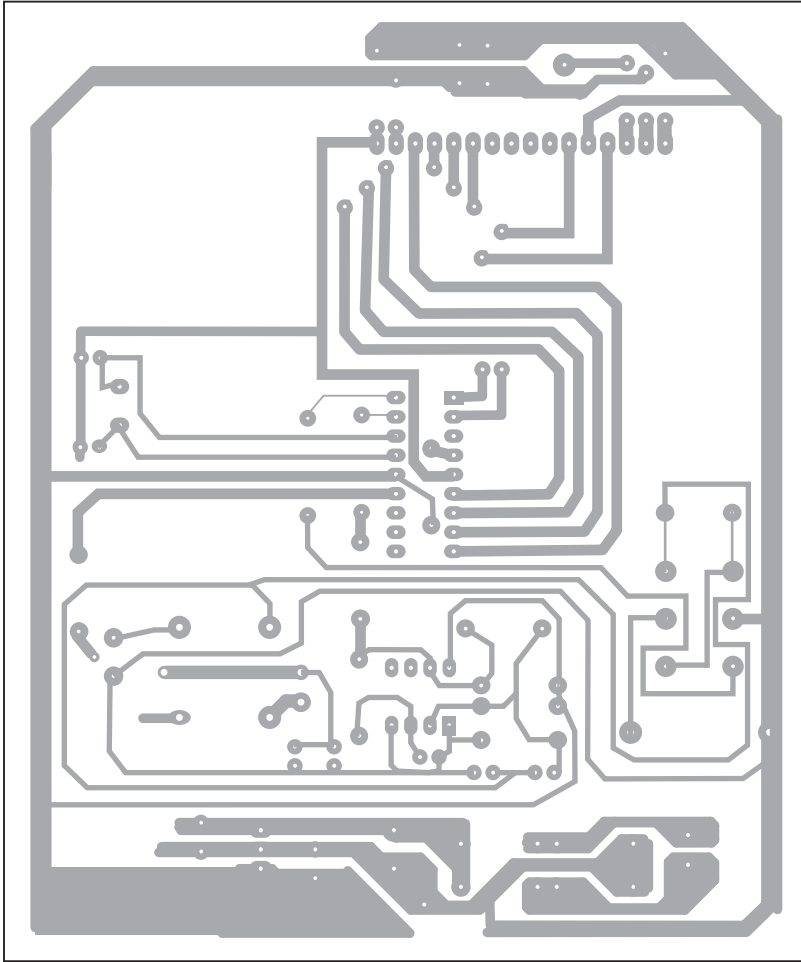


Fig.3 : PCB Layout of Microcontroller Based Inductance Capacitance Meter.

```

movlw b'00001000'
movwf porta
movlw lcd7_0
movwf lcd70
movlw lcd7_1
movwf lcd71
movlw lcd7_2
movwf lcd72
movlw lcd7_3
movwf lcd73
movlw lcd7_4
movwf lcd74
movlw lcd7_5
movwf lcd75
movlw lcd7_6
movwf lcd76
movlw lcd7_7
movwf lcd77
movlw lcd7_8
movwf lcd78
movlw lcd7_9
movwf lcd79
clrf c10s
clrf c01s
bsf time_f,0
stand_by:

```

```

        bcf porta,ra0
        bcf porta,ra1
        bcf porta,ra2
        #ifndef_debug
        call t1m
        btfsc portb,rb6
        goto stand_by
        #endif
Start:
        bcf porta,ra3
        #ifndef_debug
        movlw d'255'
        #else
        movlw d'43'
        #endif
        movwf tmr0
        #ifndef_debug
        movlw d'2'
        #else
        movlw d'46'
        #endif
        movwf tm_cnt
        movlw h'a0'
        movwf intcon
loop:
        call led_cont

```

```

        bsf status,rp0
        movlw h'ff'
        movwf trisb
        bcf status,rp0
        bcf porta,ra0
        bcf porta,ra1
        bcf porta,ra2
        #ifndef_debug
        movlw h'fe'
        #else
        call t1m
        movf portb,w
        #endif
        xorlw h'ff'
        andlw h'0f'
        movwf c10m
        bsf porta,ra0
        #ifndef_debug
        movlw h'ff'
        #else
        call t1m
        movf portb,w
        #endif
        xorlw h'ff'
        andlw h'0f'
        movwf c01m
        call led_cont
        movf c10m,w
        btfss status,z
        goto sw_check
        movf c01m,w
        btfsc status,z
        goto stand_by
sw_check:
        bsf status,rp0
        bsf trisb,rb6
        bcf status,rp0

```

CONSTRUCTION

```
movf time_f,w
btfsc status,z
goto time_out
#ifndef debug
    btfsc porta,ra4
#endif
    goto loop
time_out
    clrf intcon
goto init
bsf status,rp0
clrf trisb
bcf status,rp0
bcf porta,ra0
bcf porta,ra1
bsf porta,ra2
movf c10m,w
movwf ttl_in
call ttl_7lcd
bsf porta,ra0
Movf c01m,w
movwf ttl_in
call ttl_7lcd
bcf porta,ra0
bsf porta,ra1
movf c10s,w
movwf ttl_in
call ttl_7lcd
bsf porta,ra0
movf c01s,w
movwf ttl_in
call ttl_7lcd
return
ttl_7lcd
movlw lcd70
addwf ttl_in,w
movwf fsr
movf indf,w
movwf portb
#ifndef debug
call t1m
#endif
return
t1m movlw 2
movwf cnt1m
tm1lp1 movlw d'249'
movwf cnt500u
tm1lp2 nop
nop
decfsz cnt500u,f
goto tm1lp2
decfsz cnt1m,f
goto tm1lp1
return
int:
goto tm1lp2
decfsz cnt1m,f
goto tm1lp1
return
int:
movwf w_save
movf status,w
movwf s_save
```

```
bcf status,rp0
btfsc intcon,t0if
goto timer_int int_end
movf s_save,w
movwf status
swapf w_save,f
swapf w_save,w
reftie timer_int:
bcf intcon,t0if
#ifndef debug
movlw d'255' #else
movlw d'43' #endif
movwf tmr0
decfsz tm_cnt,f
goto int_end #ifndef debug
movlw d'2' #else
movlw d'46' #endif
movwf tm_cnt
decfsz c01s,w
goto countdown
movf c10s,w
btfss status,z
goto countdown
movf c01m,w
btfss status,z
goto countdown
movf c10m,w
btfss status,z
goto countdown
time_out1:
clrf time_f
goto int_end
movf c01s,w
btfss status,z
goto cd_c01s
movlw 9
movwf c01s
movf c10s,w
btfss status,z
goto cd_c10s
movlw 5
movwf c10s
movf c01m,w
btfss status,z
goto cd_c01m
movlw 9
movwf c01m
movf c10m,w
btfss status,z
goto cd_c10m
goto time_out1
cd_c01s:
decf c01s,f
goto int_end
cd_c10s:
decf c10s,f
goto int_end
cd_c01m:
decf c01m,f
goto int_end
cd_c10m:
decf c10m,f
goto int_end
End
```